

Digital Logic Design



Hajar Falahati

Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir



Multiplexer (MUX)

 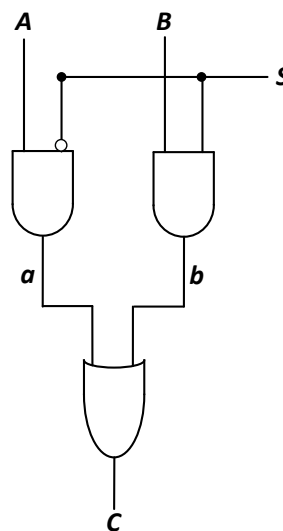- **Selects** one of the N inputs to connect it to the output
- Needs $\log_2 N$ -bit control input
- 2:1 MUX
- How is it useful?



DeMultiplexer (DeMUX)

  - **Selects** one of the N outputs and send the data
- Needs $\log_2 N$ -bit control input
- **1** input and 2^n output lines



Outline

- Binary Arithmetic Units
 - Adder
 - Subtractor
 - Comparator



Adder

Half Adder (HA)

- Inputs


- 2 1-bit numbers
- x_i, y_i

- Output

- 1 1-bit number
 - A.k.a., sum (s_i)
- 1 1-bit number
 - A.k.a., carry (c_i)


- Functionality

- Add two numbers

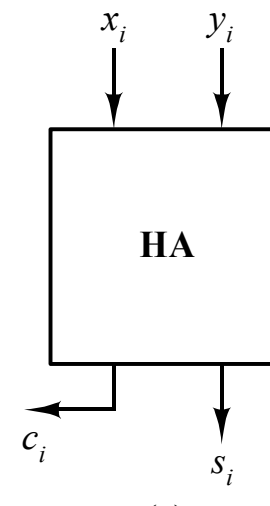

$$\begin{array}{r}
 x_i \\
 + y_i \\
 \hline
 c_i \ s_i
 \end{array}$$

Half Adder (cont'd)

 

$$\begin{array}{r} x_i \\ + y_i \\ \hline c_i \ s_i \end{array}$$

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \ 0 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 0 \ 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 0 \\ \hline 0 \ 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 1 \ 0 \end{array}$$

x_i	y_i	c_i	s_i
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


S		Y
	0	1
X	1	3

C		Y
	0	1
X	2	1

$$s_i = \bar{x}_i \cdot y_i + x_i \cdot \bar{y}_i$$

$$c_i = x_i \cdot y_i$$



Half Adder (cont'd)

 

$$\begin{array}{r} x_i \\ + y_i \\ \hline c_i \quad s_i \end{array}$$

$$s_i = \bar{x}_i \cdot y_i + x_i \cdot \bar{y}_i$$

$$c_i = x_i \cdot y_i$$

  

Full Adder (FA)

- Inputs


- 2 1-bit numbers
 - x_i, y_i
- 1 1-bit number
 - c_{in} or c_{i-1}

- Output

- 1 1-bit number
 - A.k.a., sum (s_i)
- 1 1-bit number
 - A.k.a., carry (c_i)


- Functionality

- Add two numbers

 

$$\begin{array}{r}
 c_{i-1} \\
 x_i \\
 + y_i \\
 \hline
 c_i \ s_i
 \end{array}$$

Full Adder (cont'd)

 

		1	1	1	1
x_i		0	0	1	1
$+ y_i$		$+ 0$	$+ 1$	$+ 0$	$+ 1$
$c_i \ s_i$		0 1	1 0	1 0	1 1

x_i	y_i	c_{i-1}	c_i	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

		x_i			
		$x_i y_i$			
		00	01	11	10
c_{i-1}	0	0	1	0	1
c_{i-1}	1	1	0	1	0
		y_i			

		x_i			
		$x_i y_i$			
		00	01	11	10
c_{i-1}	0	0	0	1	0
c_{i-1}	1	0	1	1	1
		y_i			

Full Adder (cont'd)

$$s_i = \bar{x}_i \cdot y_i \cdot \bar{c}_{i-1} + x_i \cdot \bar{y}_i \cdot \bar{c}_{i-1} + x_i \cdot y_i \cdot c_{i-1} + \bar{x}_i \cdot \bar{y}_i \cdot c_{i-1}$$

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$

		x_i			
		y_i			
		00	01	11	10
c_{i-1}	0	0	2	6	4
	1	1	3	7	5

Diagram showing the truth table for the Sum (s_i) and Carry-out (c_i) of a Full Adder. The inputs are x_i , y_i , and c_{i-1} . The outputs are s_i and c_i . The table is a 2x4 grid with c_{i-1} as the row header and $x_i y_i$ as the column header. The values in the cells represent the decimal indices for the minterms. The sum s_i is 1 for minterms 0, 2, 4, and 6. The carry-out c_i is 1 for minterms 3, 5, 6, and 7.

		x_i			
		y_i			
		00	01	11	10
c_{i-1}	0	0	2	6	4
	1	1	3	7	5

Diagram showing the truth table for the Sum (s_i) and Carry-out (c_i) of a Full Adder. The inputs are x_i , y_i , and c_{i-1} . The outputs are s_i and c_i . The table is a 2x4 grid with c_{i-1} as the row header and $x_i y_i$ as the column header. The values in the cells represent the decimal indices for the minterms. The sum s_i is 1 for minterms 0, 2, 4, and 6. The carry-out c_i is 1 for minterms 3, 5, 6, and 7.

$$c_o = x_i \cdot y_i + y_i \cdot c_{i-1} + x_i \cdot c_{i-1}$$

$$c_o = x_i \cdot y_i + (x_i + y_i) \cdot c_{i-1}$$



$$c_i = x_i \cdot y_i + (x_i \oplus y_i) \cdot c_{i-1}$$

Full Adder (cont'd)





$$s_i = \bar{x}_i \cdot y_i \cdot \bar{c}_{i-1} + x_i \cdot \bar{y}_i \cdot \bar{c}_{i-1} + x_i \cdot y_i \cdot c_{i-1} + \bar{x}_i \cdot \bar{y}_i \cdot c_{i-1}$$

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$


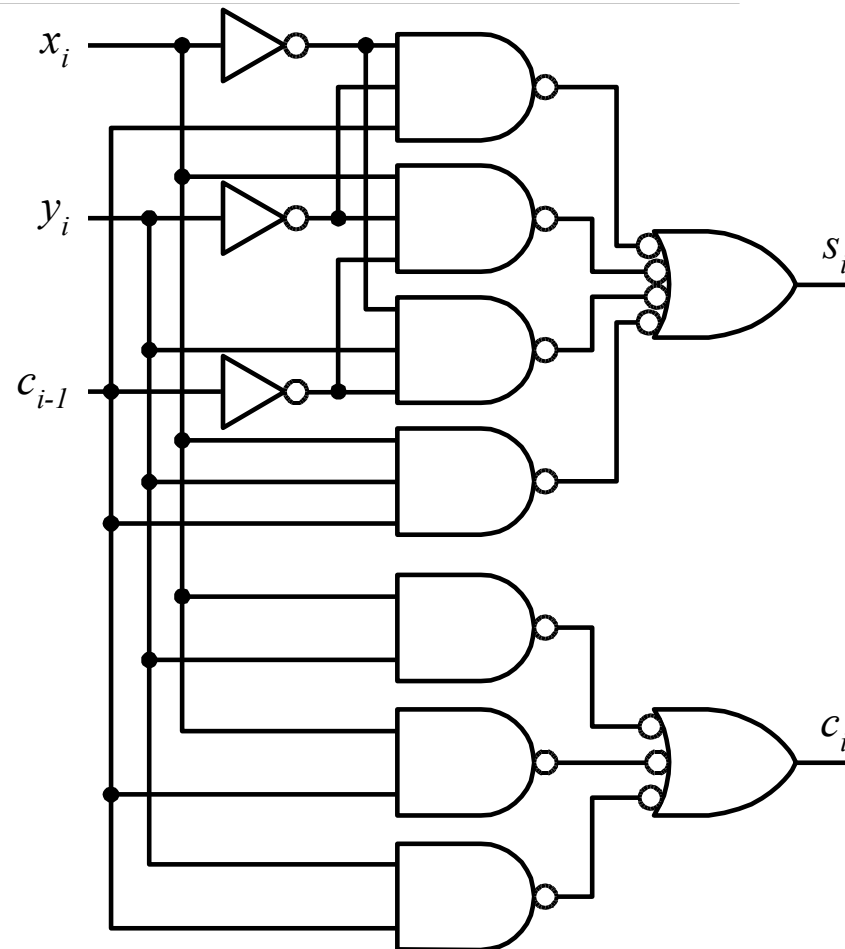
 
$$c_i = x_i \cdot y_i + y_i \cdot c_{i-1} + x_i \cdot c_{i-1}$$



Full Adder Vs. Half Adder

   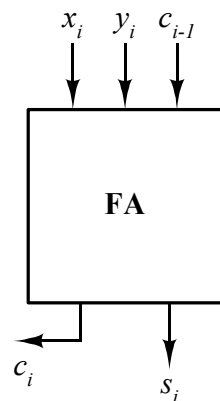

Full Adder Vs. Half Adder(cont'd)

   

Binary Adder

- Add N-bit Numbers
- Add Two vectors


			FA
	1 00010	1 00010	
0	11101	11101	
11101			
+ 10001	+ 10001	+ 10001	
	1 01110	1 01110	

Binary Adder

- Add N-bit Numbers
- Add Two vectors



FA

1	0	0	0	1	0
	1	1	1	0	1
+	1	0	0	0	1
1	0	1	1	1	0

 

Ripple Carry Adder



Ripple-Carry-Adder (RCA)

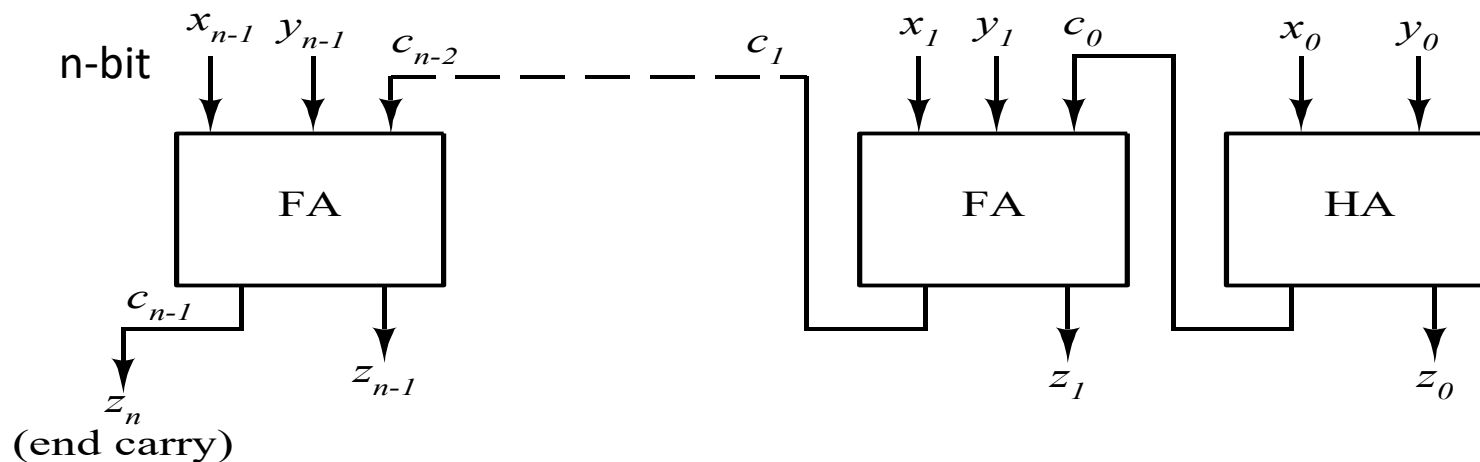 

Delay Analysis

- Propagation **delay** through a typical logic gate
 - t_{gate}
- Calculate the **delay** of n-bit Ripple carry Adder
 - ?


Delay Analysis: HA

  

$$t_{\text{add}} = 3 t_{\text{gate}}$$


$$t_{\text{carry}} = 2 t_{\text{gate}}$$

Delay Analysis: FA

 


$$t_{\text{add}} = 3 t_{\text{gate}}$$

$$t_{\text{carry}} = 2 t_{\text{gate}}$$

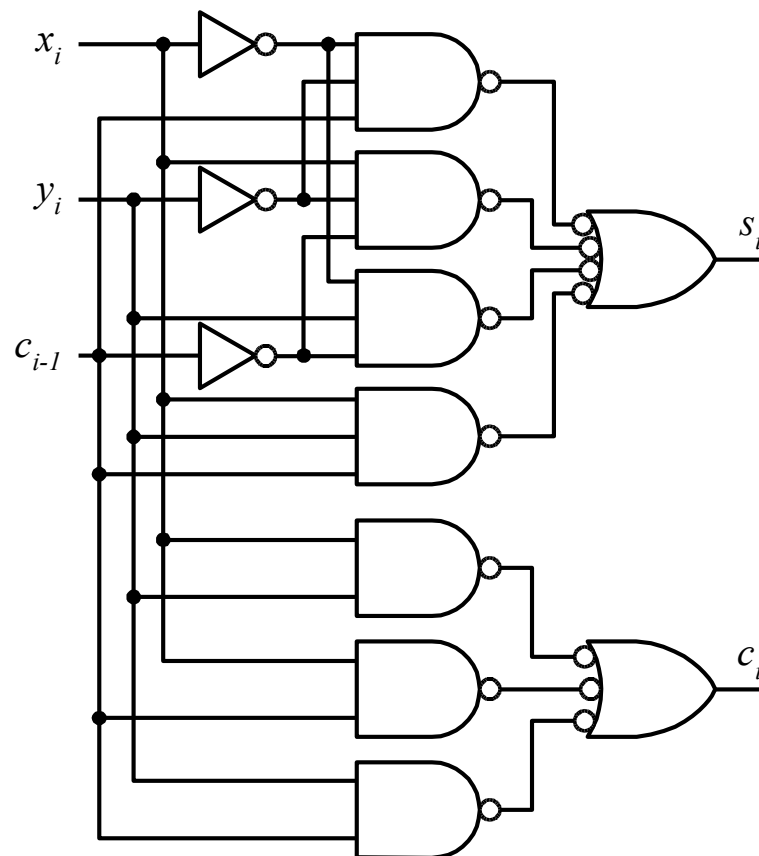

Delay Analysis: Ripple-Carry-Adder

	delay
S_0	3
C_0	2
S_1	$5 = 3+2$
C_1	$4 = 2+2$
S_2	$7 = 3+4$
C_2	$6 = 2+4$
S_3	$9 = 3+6$
C_3	$8 = 2+6$

 


$$t_{\text{add}} = 3 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = (2n + 1) t_{\text{gate}}$$

$$t_{\text{carry}} = 2 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = 2n t_{\text{gate}}$$

Delay Analysis: Ripple-Carry-Adder (cont'd)

 - Each bit adder **waits** for its carry input
 - Generate and propagate carry
- Carry propagation**
- => **long sequential wait chain**
- => Ripple-carry-adder is **slow**




$$t_{\text{add}} = 3 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = (2n + 1) t_{\text{gate}}$$

$$t_{\text{carry}} = 2 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = 2n t_{\text{gate}}$$

Faster Binary Adder

 - Can we make **ripple-carry-adder** faster?
- Can we generate all terms in **parallel**?
- Can we say anything about Cout **without** having Cin?



$$t_{\text{add}} = 3 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = (2n + 1) t_{\text{gate}}$$

$$t_{\text{carry}} = 2 t_{\text{gate}} + (n-1) 2 t_{\text{gate}} = 2n t_{\text{gate}}$$

Faster Binary Adder (cont'd)

$$s_i = x_i \oplus y_i \oplus c_{i-1}$$


$$c_i = x_i \cdot y_i + (x_i \oplus y_i) \cdot c_{i-1}$$

$g_i = x_i \cdot y_i$: Carry generate (G)

$p_i = (x_i \oplus y_i)$: Carry propagate (P)

$$s_i = p_i \oplus c_{i-1}$$

$$c_i = g_i + p_i \cdot c_{i-1}$$

 

Carry Look Ahead

• Inputs



- 2 1-bit numbers
 - x_i, y_i
- 1 1-bit number
 - c_{in} or c_{i-1}

• Output

- 1 1-bit number
 - A.k.a., **sum** (s_i)
- 1 1-bit number
 - A.k.a., **carry propagate** (p_i)
- 1 1-bit number
 - A.k.a., **carry generate** (g_i)

$$g_i = x_i \cdot y_i$$

$$p_i = (x_i \oplus y_i)$$

  

Carry Look Ahead (cont'd)

$$s_i = p_i \oplus c_{i-1}$$

$$c_i = g_i + p_i \cdot c_{i-1}$$

$$c_0 = g_0 + p_0 c_{in}$$

$$s_0 = p_0 \oplus c_{in}$$

$$c_1 = g_1 + p_1 c_0$$

$$= g_1 + p_1 g_0$$



$$s_1 = p_1 \oplus c_0$$

$$c_2 = g_2 + p_2 c_1$$

$$= g_2 + p_2 (g_1 + p_1 g_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0$$

$$s_2 = p_2 \oplus c_1$$


 
 


Carry Look Ahead: Delay

$$t_g = t_p = t_{\text{gate}}$$

$$t_c = 2 t_{\text{gate}}$$

	Delay	Total Delay
p_i	1	1
g_i	1	1
S_0	1	
C_0	2	
S_1	1	
C_1	2	
S_2	1	
C_2	2	

 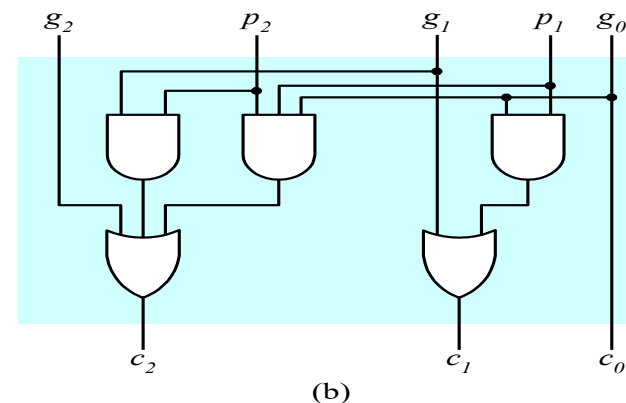 




$$s_i = p_i \oplus c_{i-1} \quad c_i = g_i + p_i \cdot c_{i-1}$$

Carry Look Ahead: Delay (cont'd)

$$t_g = t_p = t_{\text{gate}}$$

$$t_c = 2 t_{\text{gate}}$$

	Delay	Total Delay
p_i	1	1
g_i	1	1
S_0	1	
C_0	2	3
S_1	1	
C_1	2	3
S_2	1	
C_2	2	3

   




$$s_i = p_i \oplus c_{i-1} \quad c_i = g_i + p_i \cdot c_{i-1}$$

Carry Look Ahead: Delay (cont'd)

$$t_g = t_p = t_{\text{gate}}$$

$$t_c = 2 t_{\text{gate}}$$

	Delay	Total Delay
p_i	1	1
g_i	1	1
S_0	1	4
C_0	2	3
S_1	1	4
C_1	2	3
S_2	1	4
C_2	2	3

   

$$s_i = p_i \oplus c_{i-1} \quad c_i = g_i + p_i \cdot c_{i-1}$$

Carry Look Ahead: Delay (cont'd)

- Adder module

- $t_g = t_p = t_{\text{gate}}$




- CLA module

- $t_c = 2 t_{\text{gate}}$

- Total

- $t_{\text{add}} = t_{\text{gate}} + 2 t_{\text{gate}} + t_{\text{gate}} = 4 t_{\text{gate}}$

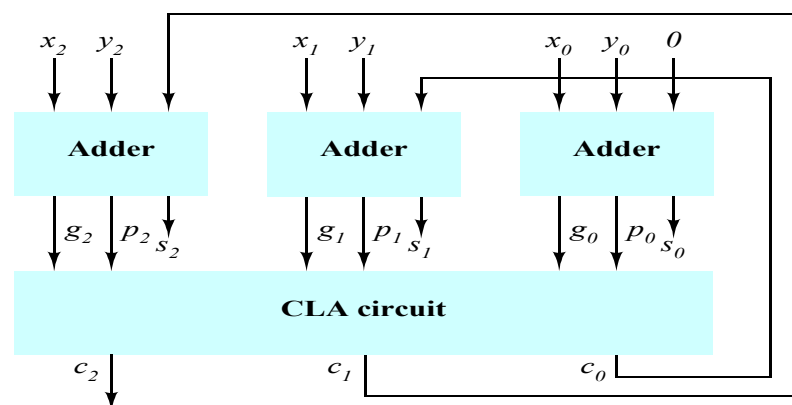  - $t_{\text{carry}} = t_{\text{gate}} + 2 t_{\text{gate}} = 3 t_{\text{gate}}$



$$s_i = p_i \oplus c_{i-1} \quad c_i = g_i + p_i \cdot c_{i-1}$$


Carry Look Ahead: Delay (cont'd)

- Adder module


- $t_g = t_p = t_{\text{gate}}$

- CLA module

- $t_c = 0 - 2 t_{\text{gate}}$

 

(a)

 

(b)

$$c_0 = g_0 + p_0 c_{in}$$


$$s_0 = p_0 \oplus c_{in}$$

$$c_1 = g_1 + p_1 c_0$$

$$s_1 = p_1 \oplus c_0$$

$$c_2 = g_2 + p_2 c_1$$

$$s_2 = p_2 \oplus c_1$$

 


Carry Look Ahead: Delay (cont'd)


$$t_g = t_p = t_{\text{gate}}$$

$$t_c = 0 - 2 t_{\text{gate}}$$


	Delay	Total Delay
p_i	1	1
g_i	1	1
S_0	1	2
C_0	0	1
S_1	1	2
C_1	2	3
S_2	1	4
C_2	2	3

 

(a)

 

(b)

 

Carry Look Ahead: Summary

- CLA circuit can **not** be **so big**
 - Calculating **C** becomes **too long**
 - **Cannot** be evaluated in 2 gate delay
 - => **At most 4 bit**

CLA – 4

$$c_0 = g_0 + p_0 c_{in}$$

$$s_0 = p_0 \oplus c_{in}$$

$$c_1 = g_1 + p_1 c_0$$


$$s_1 = p_1 \oplus c_0$$

$$c_2 = g_2 + p_2 c_1$$

$$s_2 = p_2 \oplus c_1$$

$$c_3 = g_3 + p_3 c_2$$

$$s_3 = p_3 \oplus c_2$$

 

$$s_i = p_i \oplus c_{i-1}$$


$$c_i = g_i + p_i \cdot c_{i-1}$$

Carry Look Ahead: Long operands

- How about long operands
- Example: add two 8-bit numbers

8-bit Carry Look Ahead: Cascade

 - First design
 - Ripple carry among CLAs



8-bit Carry Look Ahead: Multi-level CLA

- Add two 8-bit numbers

CLA – 4

$$c_0 = g_0 + p_0 c_{in}$$

$$s_0 = p_0 \oplus c_{in}$$

$$c_1 = g_1 + p_1 c_0$$

$$s_1 = p_1 \oplus c_0$$

$$c_2 = g_2 + p_2 c_1$$

$$s_2 = p_2 \oplus c_1$$

$$c_3 = g_3 + p_3 c_2$$

$$s_3 = p_3 \oplus c_2$$

CLA – 4

$$c_4 = g_4 + p_4 c_3$$

$$s_4 = p_4 \oplus c_3$$

$$c_5 = g_5 + p_5 c_4$$

$$s_5 = p_5 \oplus c_4$$

$$c_6 = g_6 + p_6 c_5$$

$$s_6 = p_6 \oplus c_5$$

$$c_7 = g_7 + p_7 c_6$$

$$s_7 = p_7 \oplus c_6$$

$$c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_{in}$$

$$c_4 = g_4 + p_4 g_3 + p_4 p_3 g_2 + p_4 p_3 p_2 g_1 + p_4 p_3 p_2 p_1 g_0 + p_4 p_3 p_2 p_1 p_0 c_{in}$$

$$P = p_4 p_3 p_2 p_1 p_0$$

$$G = g_4 + p_4 g_3 + p_4 p_3 g_2 + p_4 p_3 p_2 g_1 + p_4 p_3 p_2 p_1 g_0$$


$$c_4 = G + P c_{in}$$

$$c_4 = G_0 + P_0 c_{in}$$


Multi-level CLA

- CLA_1 takes the P, G 's from CLA_0 and C_{in} to generate C_4 ("seed C's")
 - 2 gate delay
 - $c_4 = G + P c_{in}$

CLA_1

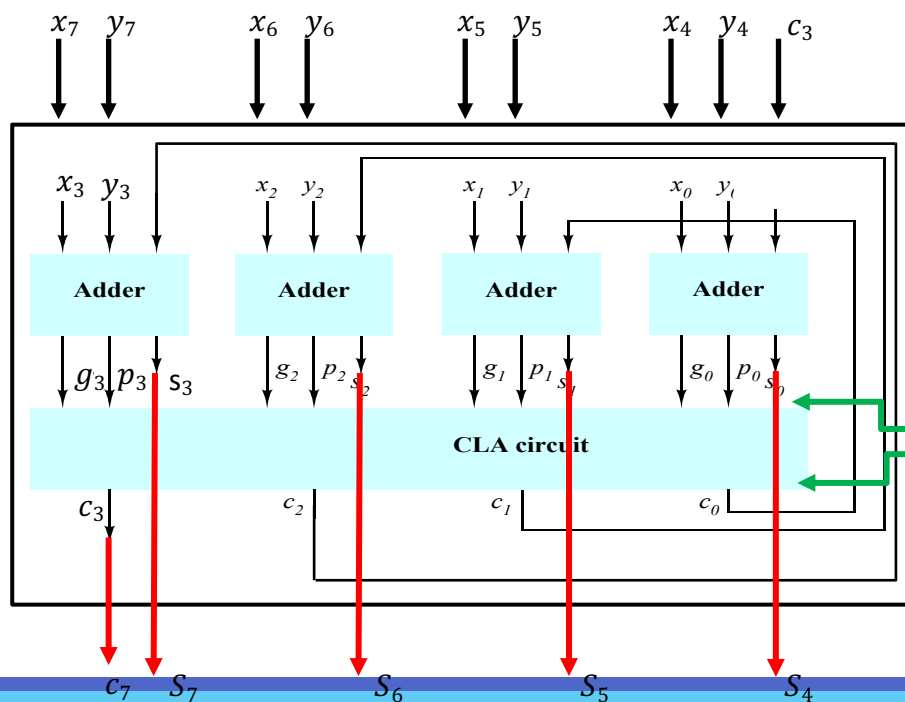

CLA_0

 


Multi-level CLA: More Detail

- Generate p_i and g_i
- Generate P_0 and G_0
- Generate C_i
- Generate S_i : t_{gate}
 - $c_4 = G + P c_{\text{in}}$

$$P = p_4 p_3 p_2 p_1 p_0$$

$$G = g_4 + p_4 g_3 + p_4 p_3 g_2 + p_4 p_3 p_2 g_1 + p_4 p_3 p_2 p_1 g_0$$

$$c_4 = G_0 + P_0 c_{\text{in}}$$

 

Thank You

